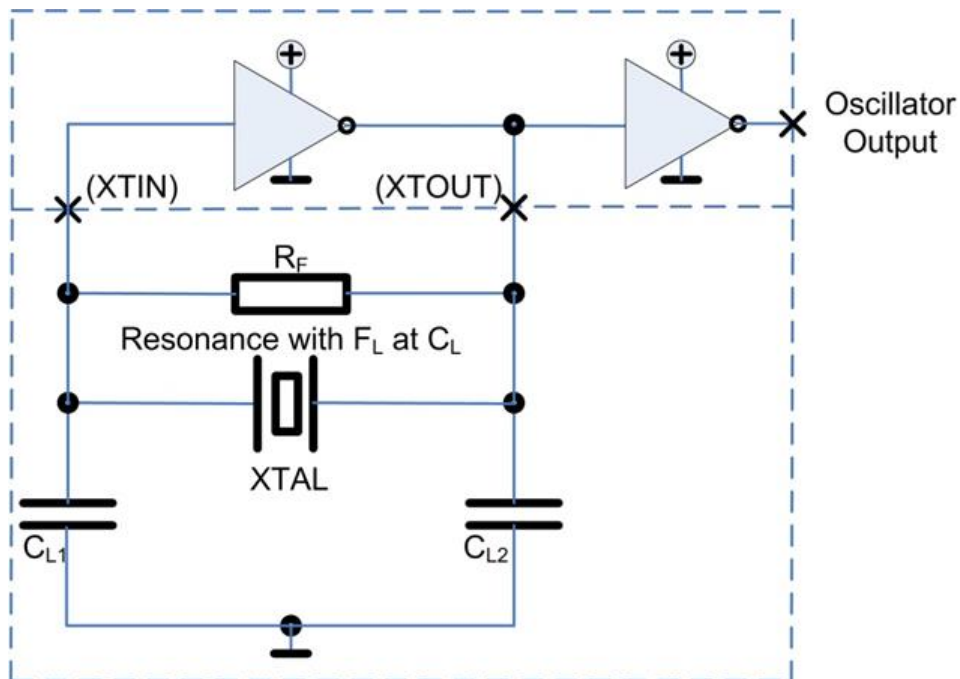


Oscillator Basics


What's the difference between a crystal and an oscillator?

- Crystal:
 - Passive component
 - Needs external energy to oscillate
- Oscillator:
 - Active component
 - Requires supply voltage
 - Is able to provide subsequent circuits with signals




Oscillation circuit

- Resonant loop:
 - Crystal (XTAL) and load capacitors (CL1 & CL2)
 - Frequency is influenced by load capacitors
 - Series resistance of the crystal is responsible for the main energy loss
- Feedback loop:
 - Includes an amplifier that amplifies signals from XTIN to XTOUT with a certain gain
 - Amplifier is needed for compensation of resonant loop loss
 - In the case of a loss factor of 0.5, the amplification has to be min. 2 to compensate
 - Additional demand: proper phase shift of the fed back signal

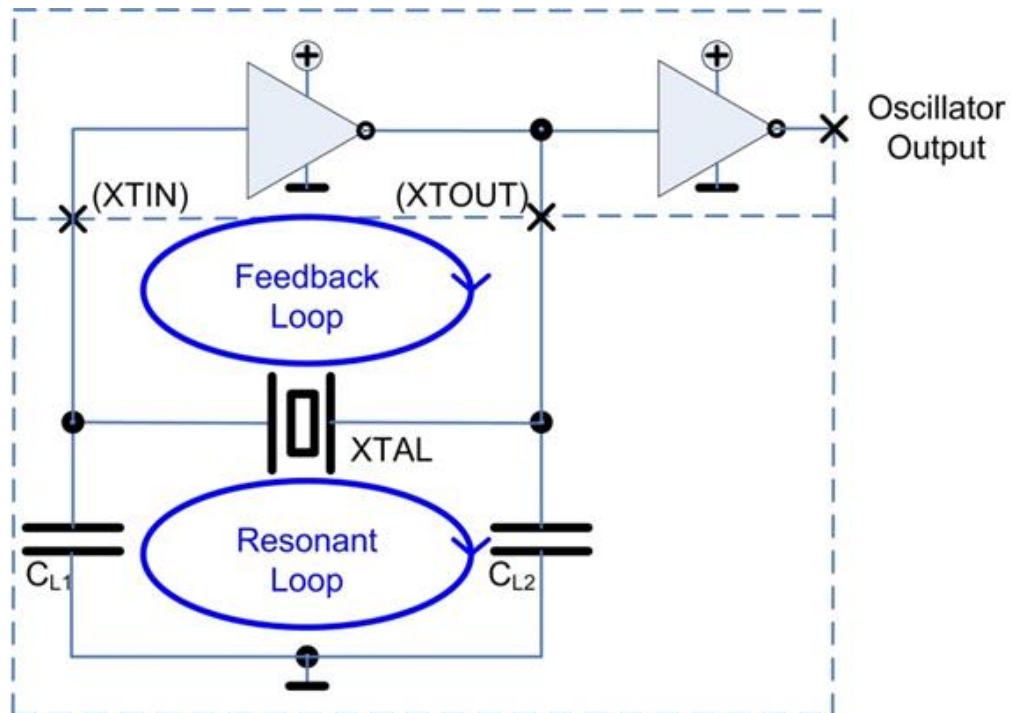


Oscillation Circuit – Output Buffer

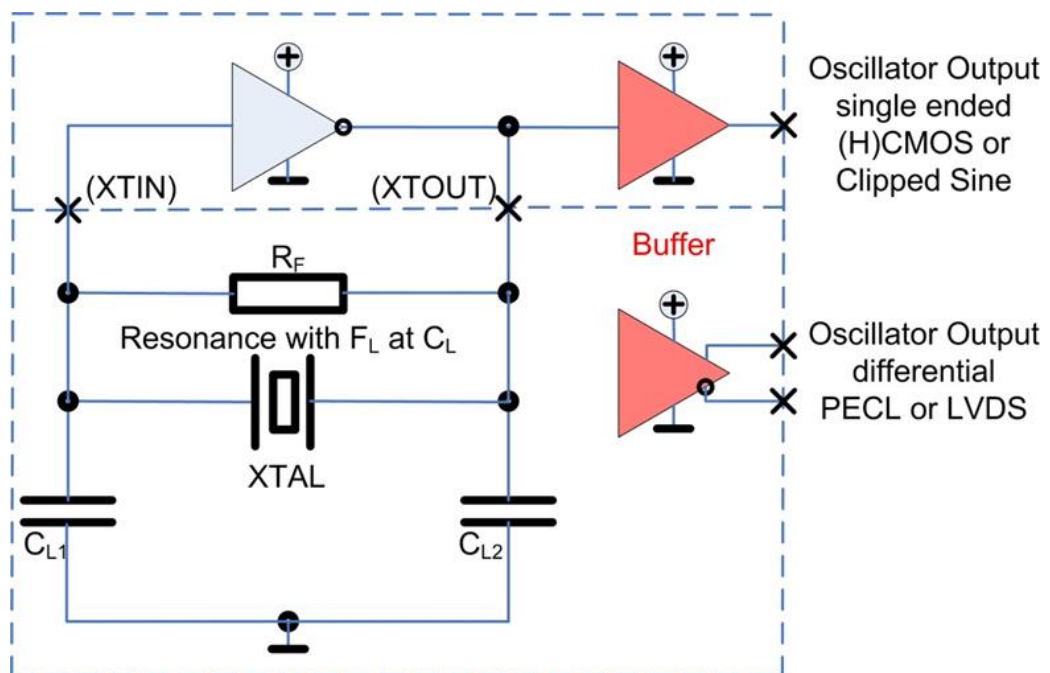
- Output buffer:
 - Isolation of the inner oscillation circuit from the external load of the external customer circuit
 - Different buffer types for the required signal types and circuit conditions
 - Single ended standard signal types: (H)CMOS, Clipped Sine
 - Differential standard signal types: PECL, LVDS



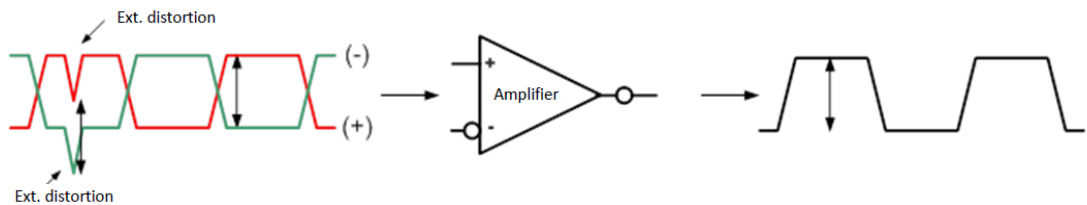- Advantages of differential buffers at high frequencies:
 - High suppression of coupled in distortion signals



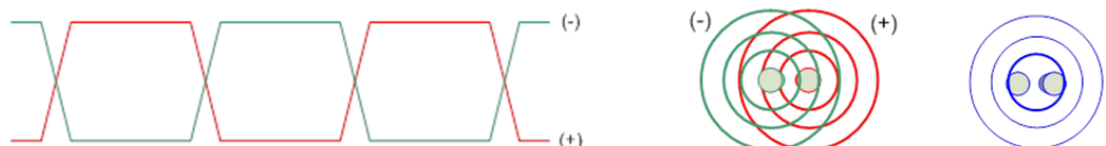- Lower undesired RF emissions produced by differential wiring



Oscillator Basics

- In comparison to single wiring (single ended buffer)




Oscillation Circuit – Stop and TriState

- Standard → Stop (with TriState), low current consumption when disabled
- Optional → TriState (only), very short startup time


| Difference of Standby Modes in Jauch Oscillators | | |
|---|--|---|
| Short Description | "TRI = Tristate only" | "STP = Stop with Tristate" |
| Explanation | during standby: Oscillating stage operates & Output has Tristate® function | during standby: Oscillating stage stops & Output has Tristate® function |
| Standby function "Disabled" signal output disabled | <p>Example values: Oscillator Power, $V_{DD} = 5V$ Current Consumption = reduced (3mA) E/D = 0V (Logic Low) Output = no signal, high impedance Oscillation Circuit = fully enabled Output Circuit = disabled</p> | <p>Example values: Oscillator Power, $V_{DD} = 5V$ Current Consumption = almost Zero (some μA) E/D = 0V (Logic Low) Output = no signal, high impedance Oscillation Circuit = disabled Output Circuit = disabled</p> |
| Standby function "Enabled" signal output active | <p>Example values: Oscillator Power, $V_{DD} = 5V$ Current Consumption = 10 mA E/D = 5V (Logic High or Open) Output = active (clock signal) Oscillation Circuit = fully enabled Output Circuit = enabled Enable Time $\leq 250\text{ns}$</p> | <p>Example Values: Oscillator Power, $V_{DD} = 5V$ Current Consumption = 10 mA E/D = 5V (Logic High or Open) Output = active (clock signal) Oscillation Circuit = fully enabled Output Circuit = enabled Enable Time = 1...10msec.</p> |
| Application | output multiplexed applications, <u>fast</u> reaction of output reduced power consumption when disabled | battery powered applications, power consumption <u>very low when disabled</u> , <u>slow</u> reaction of output |

Oscillator – Features Overview

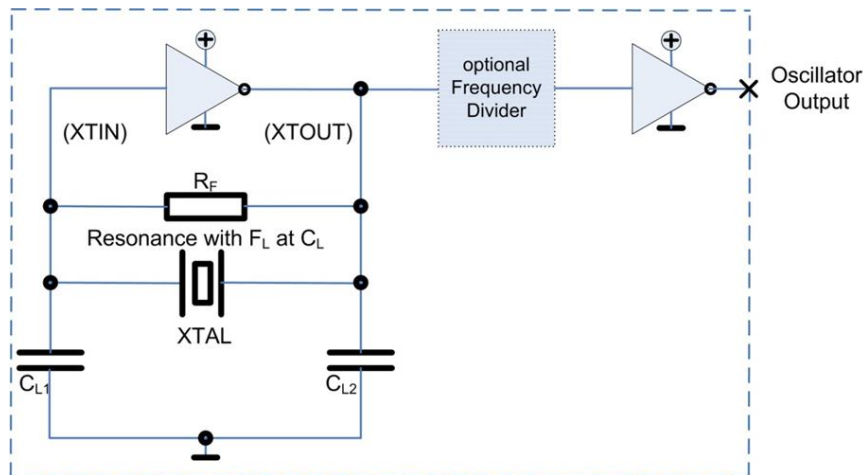- XO (Crystal Oscillator):
 - Fixed frequency oscillator (e.g. JOxx, VX3)
 - Crystal (XTAL) and Load capacitors (CL1 and CL2)
 - Resonant frequency is controlled by crystal with fixed load capacitors
 - Crystal blanks depending on the frequency at fundamental or overtone
 - Low frequencies by divider /2; /4; /8; /16; /32; /64 of the fundamental frequency




- VCXO (Voltage Controlled Crystal Oscillator):
 - Oscillator with variable frequency (e.g. JVxx)
 - Frequency variation is voltage controlled
 - Crystal (XTAL) and variable load capacitors / capacitance diodes (CL1 and CL2)
 - Resonant frequency is controlled by crystal and variable capacitors
 - Fundamental crystal blanks only (frequency at 3rd overtone not pullable => unusable)
 - Low frequencies by divider /2; /4; /8; /16; /32; /64 of the fundamental frequency

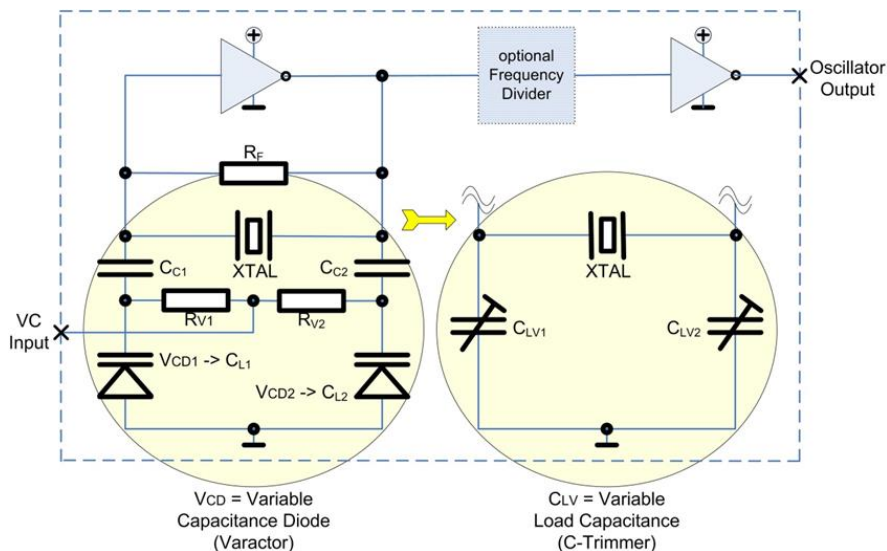


Oscillator Basics

- TCXO “light” (Temperature Compensated Crystal Oscillator):
 - Temperature compensated Oscillator (JOxxH), better stability than JOxx
 - Crystal and variable load capacitors / capacitance diodes (varactors)
 - Resonant frequency is controlled by crystal and fixed load capacitors
 - Compensation with stored compensation values, according to current temperature
 - Compensation table determined and stored by calibration in production process
 - Fundamental crystal blanks only (frequency at 3rd overtone not pullable => unusable)

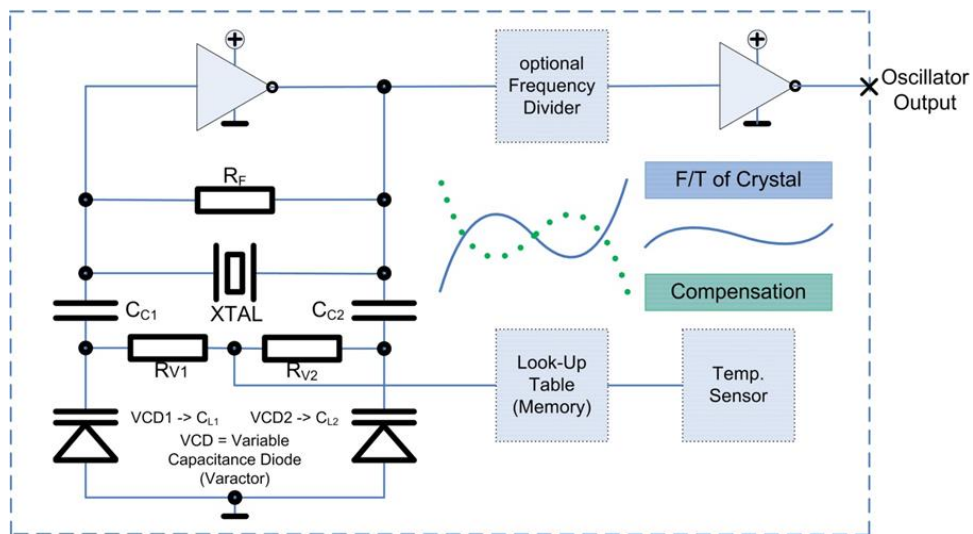


- TCXO (Temperature Compensated Crystal Oscillator):
 - Temperature Stabilized Oscillator with high stability (JTxx, JTxxC)
 - Variant with variable frequency optionally available as JTxxV (-> VCTCXO)
 - Crystal and variable load capacitors / capacitance diodes (varactors)
 - Resonant frequency is controlled by crystal and variable load capacitors
 - Compensation with saved compensation values, fitting to current temperature
 - Compensation table determined and stored by calibration in production process
 - Fundamental crystal blanks only (frequency at 3rd overtone not pullable => unusable)

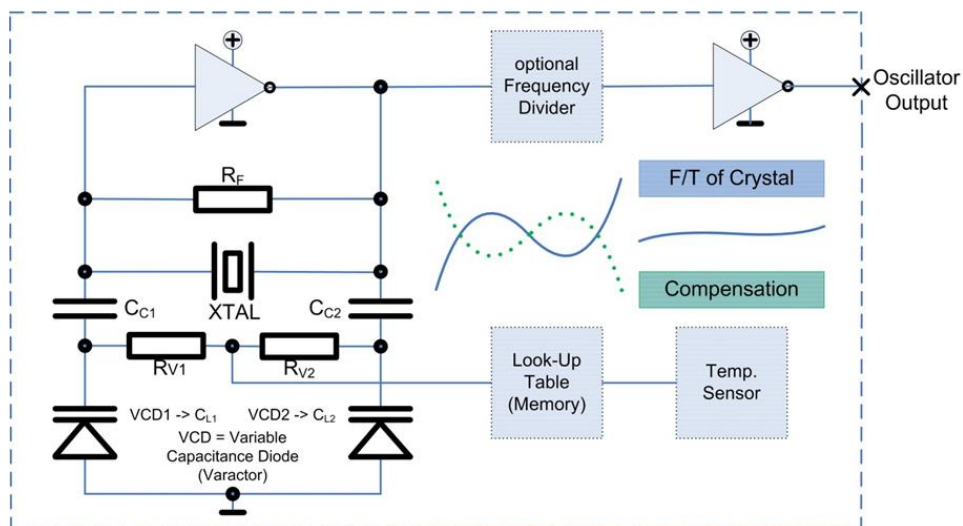


MEMS vs. Crystal Oscillator – Block Diagram Comparison

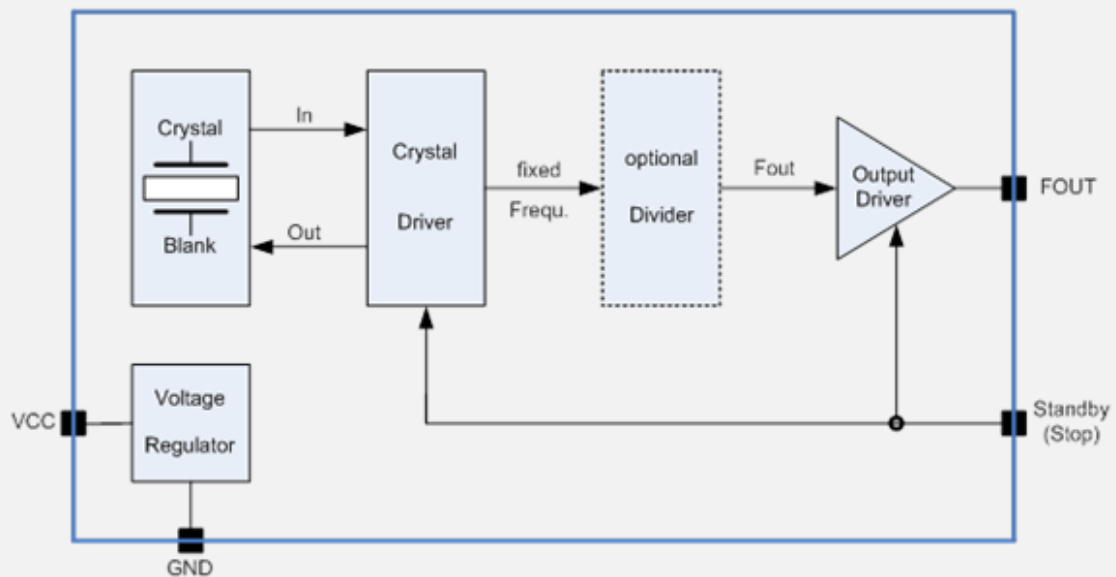Crystal oscillator (blank determines frequency)




Crystal programmable oscillator

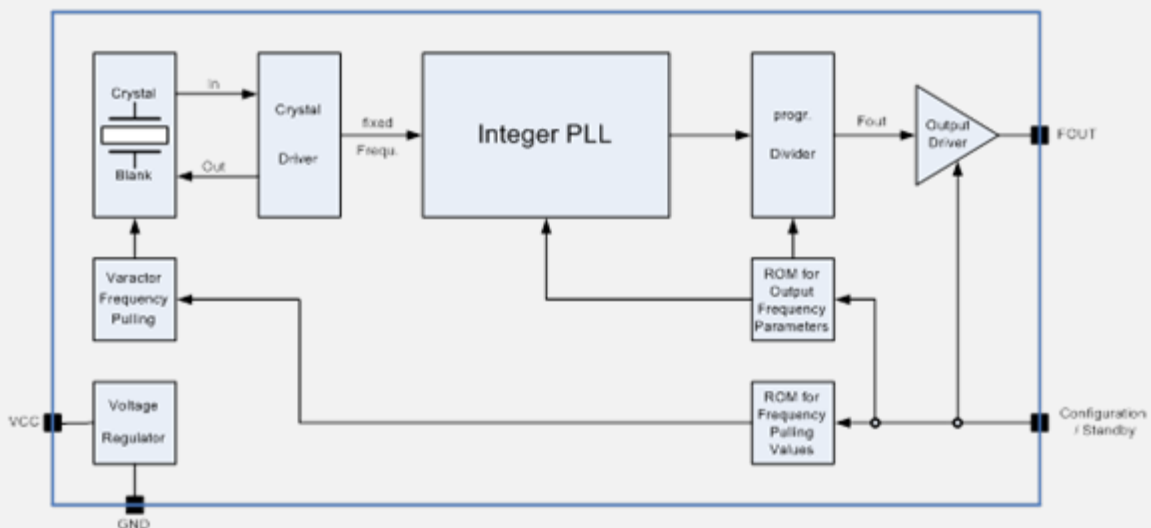

MEMS oscillator

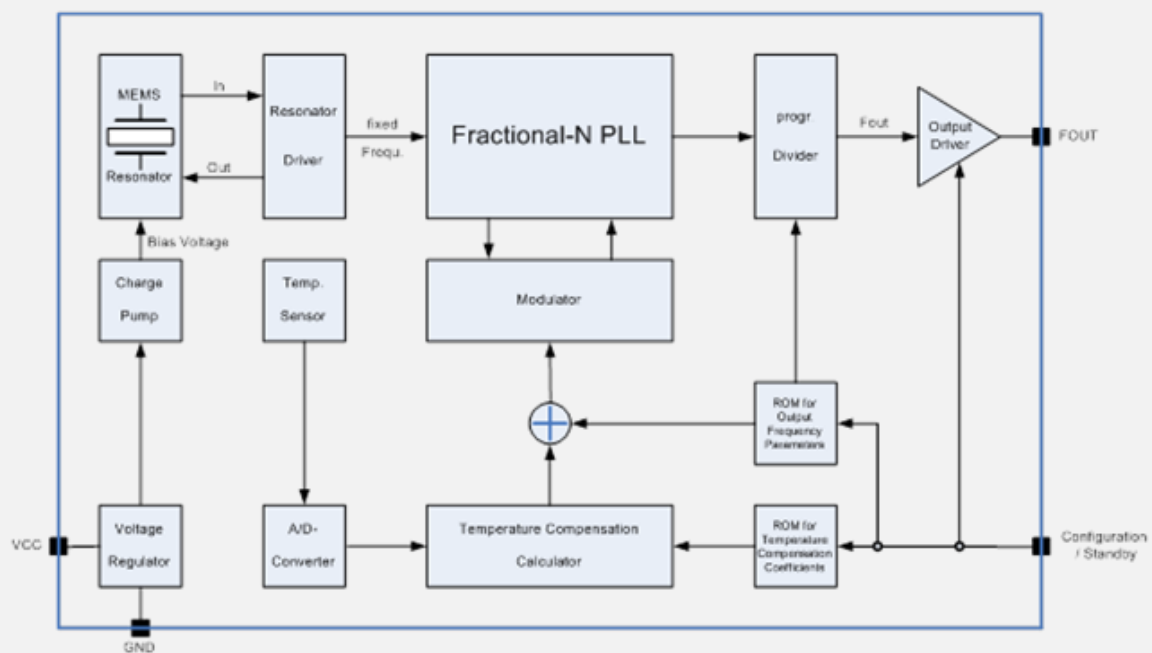- ASIC contains
 - Temperature sensor
 - Fractional N PLL
 - Configurable algorithm for temperature compensation
 - Memory for compensation coefficients



Oscillators – Features Overview

- Programmed Oscillator:
 - Oscillator with programmed output frequency
 - Could be crystal based or MEMS based
- Programmed Crystal Oscillator (XO):
 - Blank part contains crystal with fixed frequency and programmable IC
 - Customer frequency by division ($/ R$) und multiplication ($\times M$) of fixed frequency
 - Low output frequency by divider $/2$; $/4$; $/8$; $/16$; $/32$; $/64$ derived from VCO
 - Unsolvable ratios of target frequency and blank frequency possible (not programmable)
- Programmed MEMS Oscillator:
 - The blank part contains MEMS with fixed frequency and programmable ASIC
 - ASIC contains temperature sensor and mathematic algorithm to compensate the temperature dependency and frequency tolerance of the MEMS resonator
 - In addition, the ASIC contains the registers that contain the customer-specific settings like frequency, edge control or enable/disable function